


## ECE 302 - Linear System Analysis

### Homework #4

---

**Due Date:** September 24, 2025

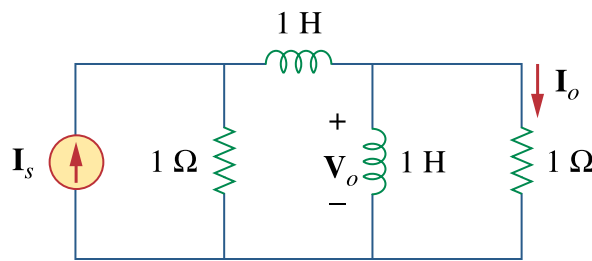1. Lathi & Green problem 2.2-6
2. Lathi & Green problem 2.2-8
3. Compute the impulse response,  $h(t)$ , for the system in the previous problem *without* using the Laplace transform.
4. Consider the circuit shown below.



- (a) Determine the input-output equation for this system, where the input is  $x = I_s$ , and the output is  $y = I_o$ .
  - (b) Compute the impulse response of the circuit,  $h(t)$ , *without* using the Laplace transform.
5. **Complex Arithmetic:** Let  $z_1 = 2 - j$  and  $z_2 = 1 + j$ . Compute the following:
- (a)  $z_1 + z_2$
  - (b)  $z_1 z_2$
  - (c)  $z_1 / z_2$

Put all your final answers in rectangular form.